

# Transmission line calculations

Weiwei Zhao

5/22/2015

Review:


Telegrapher's equation

$$\frac{\partial i}{\partial y} = -vG - \frac{\partial v_{out}}{\partial t} C$$

$$\frac{\partial v}{\partial y} = -iR - \frac{\partial i_{in}}{\partial t} L$$

$$\longrightarrow \quad \frac{v}{i} = Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}}$$
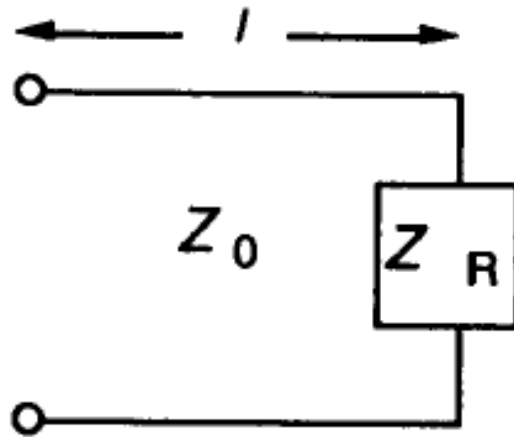
# 1. Line terminated with an arbitrary load



The impedance seen looking into a generalized transmission line terminated in  $Z_R$  is

$$Z_{in} = Z_0 \left( \frac{Z_R \cosh \gamma l + Z_0 \sinh \gamma l}{Z_0 \cosh \gamma l + Z_R \sinh \gamma l} \right) (\Omega)$$

Or

$$Z_{in} = Z_0 \left( \frac{Z_R \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_R \sin \beta l} \right)$$

where

$$\alpha = 0$$

$$\beta = \frac{2\pi}{\lambda}$$

$$\gamma = j\beta = \frac{2\pi j}{\lambda}$$

# Example: Quarter-wave line with open circuit load

What is the impedance looking into a lossless line one quarter of a wavelength long terminated in an open circuit?

$$l = \lambda / 4$$

$$Z_R = \infty \Omega$$

So from Equation (2.8.1.1):

$$Z_{in} = Z_0 \left( \frac{Z_R \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_R \sin \beta l} \right) = Z_0 \left( \frac{\infty \cos \frac{\pi}{2} + j Z_0 \sin \frac{\pi}{2}}{Z_0 \cos \frac{\pi}{2} + j \infty \sin \frac{\pi}{2}} \right)$$

$$Z_{in} = \frac{Z_0}{\infty} = 0 \Omega$$

# Example: Quarter-wave line with a generalized load

What happens when we put a general impedance  $Z_L$  at the end of a quarter wavelength line?

$$l = \lambda / 4$$

$$Z_R = Z_L$$

So again using (2.8.1.1):

$$Z_{in} = Z_0 \left( \frac{Z_R \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_R \sin \beta l} \right) = Z_0 \left( \frac{j Z_0}{j Z_L} \right) = \frac{Z_0^2}{Z_L}$$

# Example: Line terminated with short circuit

If we terminate the line in a short circuit, then

$$Z_{in} = Z_{sc} = Z_0 \left( \frac{Z_0 \sinh \gamma l}{Z_0 \cosh \gamma l} \right) = Z_0 \tanh \gamma l$$

For lossless lines, Equation (2.8.1.1) reduces to:

$$Z_{sc} = j Z_0 \tan \beta l = j Z_0 \tan \left( \frac{2\pi l}{\lambda} \right)$$


If  $\tan x$  is now approximated with  $x$  (true for small  $x$ ):

$$Z_{sc} \cong j Z_0 \beta l = j Z_0 \left( \frac{2\pi l}{\lambda} \right) = j \omega \frac{(Z_0 l)}{c}$$

$$\pi/2 < \left(\frac{2\pi l}{\lambda}\right) < \pi$$

the tangent function is negative and  $Z_{sc}$  is approximately:
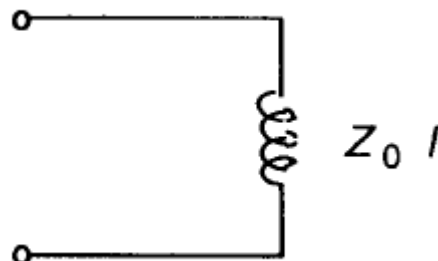
$$Z_{sc} \equiv -j Z_0 \beta l = -j Z_0 \left(\frac{2\pi l}{\lambda}\right) = -j \omega \frac{Z_0 l}{c} = \frac{1.0}{j \left(\frac{c}{\omega Z_0 l}\right)}$$



which is the impedance of a capacitor of value

$$C = \frac{1.0}{\omega^2 Z_0 l}$$

Finally, for

$$2 \pi l / \lambda = \pi / 2$$

or equivalently,

$$l = \lambda / 4$$



Summarizing our results for the short-circuited line:

$$\text{"inductive"} \begin{cases} l < \frac{\lambda}{4} \\ \frac{\lambda}{2} < l < \frac{3\lambda}{4} \end{cases}$$

$$\text{"capacitive"} \begin{cases} \frac{\lambda}{4} < l < \frac{\lambda}{2} \\ \frac{3\lambda}{4} < l < \lambda \end{cases}$$

$$\text{"series LC resonator"} \left\{ l = \frac{n\lambda}{4} \text{ where } n \in \mathbb{I} \text{ (the integers)} \right.$$