 


# Memory cells

Yifan Yuan

06/25/2021

## Transistors




CMOS


## The CMOS Inverter

logic inverters


$$Y = \overline{X}$$

 


(a)

 

(b)

 

(c)

 


(d)


**Figure 14.2** (a) Block representation of the logic inverter; (b) its CMOS realization; (c) operation when the input is a logic 1; (d) operation when the input is a logic 0.

## The Latch


basic memory element

 

(a)

 

(b)

 


(c)

**Figure 16.1** (a) Basic latch. (b) The latch with the feedback loop opened. (c) Determining the operating point(s) of the latch.

B + a positive increment  $\rightarrow$  C

 a **bistable** circuit:  $v_W$  low,  $v_X$  high,  $v_Z$  low, for a stored logic 1



## The set/reset (SR) Flip-Flop

### The Two-Input NOR Gate

$$Y = \overline{A + B} = \overline{A} \overline{B}$$

Input		Output
A	B	A NOR B
0	0	1
0	1	0
1	0	0
1	1	0


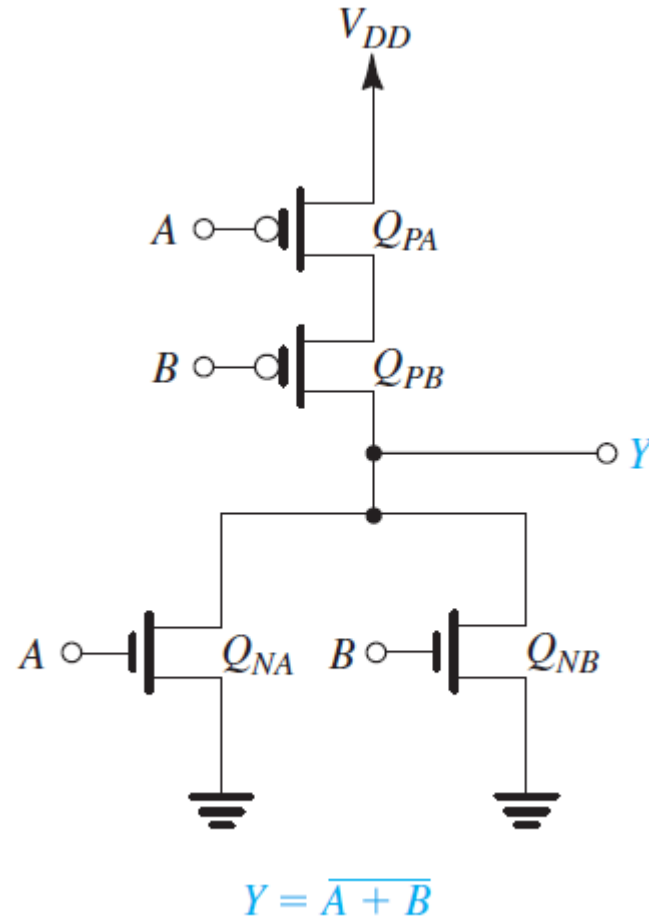



Figure 14.7 A two-input CMOS NOR gate.

A=1, B=1,  $Q_{PA}$  and  $Q_{PB}$  is OFF state,  $Q_{NA}$  and  $Q_{NB}$  is ON state, Y=0

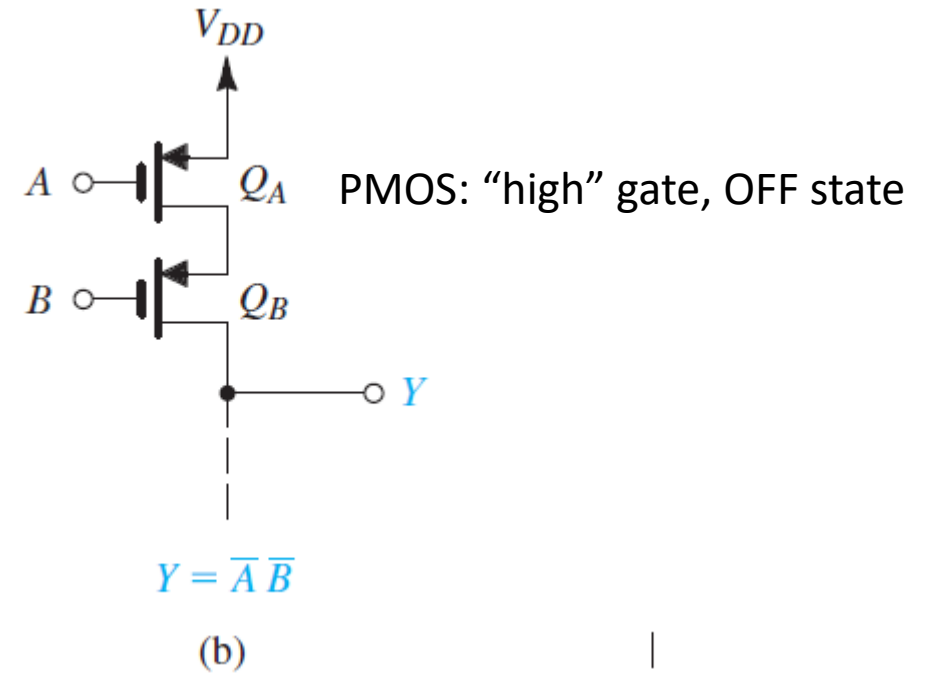A=0, B=0,  $Q_{PA}$  and  $Q_{PB}$  is ON state,  $Q_{NA}$  and  $Q_{NB}$  is OFF state, Y=1



A=1, B=1, OFF state, Y=0

 

(a)

A=1, B=1, ON state, Y=0


## The set/reset (SR) Flip-Flop

flip-flop: cross-coupling two NOR gates

### The Two-Input NOR Gate

$$Y = \overline{A + B} = \overline{A} \overline{B}$$

Input		Output
A	B	A NOR B
0	0	1
0	1	0
1	0	0
1	1	0

 

(a)

R	S	$Q_{n+1}$
0	0	$Q_n$
0	1	1
1	0	0
1	1	Not used

(b)

$G_1$  and  $G_2$  are trigger inputs of the flip-flop.

logic 1:  $Q$  is high and  $\bar{Q}$  is low

For example, when the flip-flop is storing a logic 0,  
 $Q = 0, \bar{Q} = 1$

We want to set the flip-flop as a logic 1,

Raise  $S=1$ , leave  $R=0$ ,

It forces  $\bar{Q} = 0$ , then  $Q = 1$

R	S	Q	$\bar{Q}$
0	0	0	1
0	0	1	0
1	0	0	1
0	1	1	0
1	1	0	0

*memory state*

*memory state*

logic 0

logic 1

## Memory-Chip Organization

The bits on a memory chip are addressable individually

A 64-Mbit chip needs a 26-bit address ( $2^{26} = 67,108,864 = 64\text{M}$ ).

One bit is stored in one memory cell

### A read operation:

Activate  $K$ th word line,


All cells in row  $K$  will provide contents to the bit lines,

The small readout signal is amplified and delivered to column decoder

The column decoder selects the signal of the particular column

### A write operation:

similar

 

## Random-Access Memory (RAM) Cells

two types of MOS RAM:

**Static RAMs** utilize static latches as the storage cells.

**Dynamic RAMs** store the binary data on capacitors.

static RAMs can hold their stored data indefinitely, provided the power supply remains on;

dynamic RAMs require *periodic refreshing* to regenerate the data stored on capacitors



Both static and dynamic RAMs are *volatile*; they require the continuous power supply.



## Static Memory (SRAM) Cell

a flip-flop

6T cell

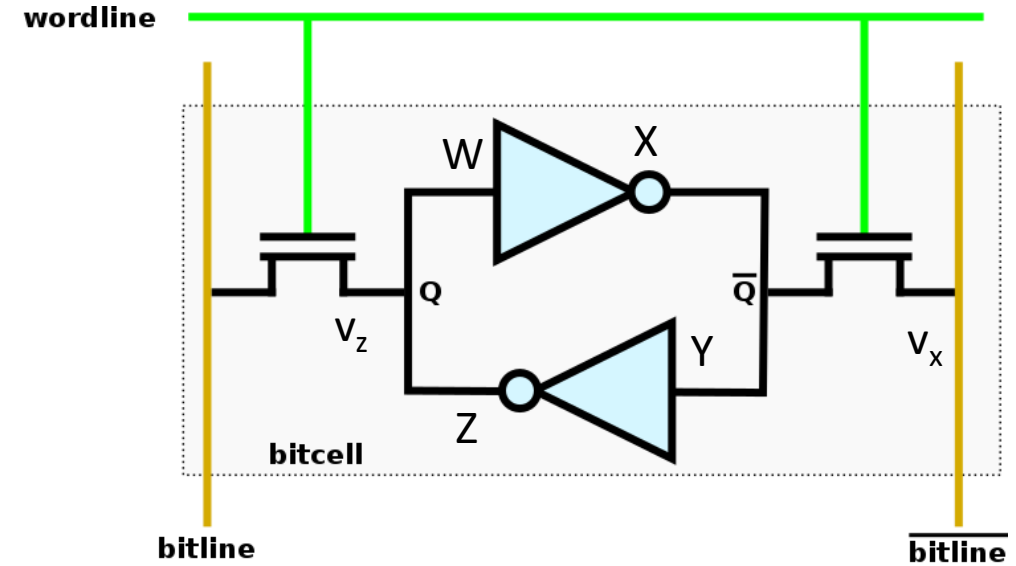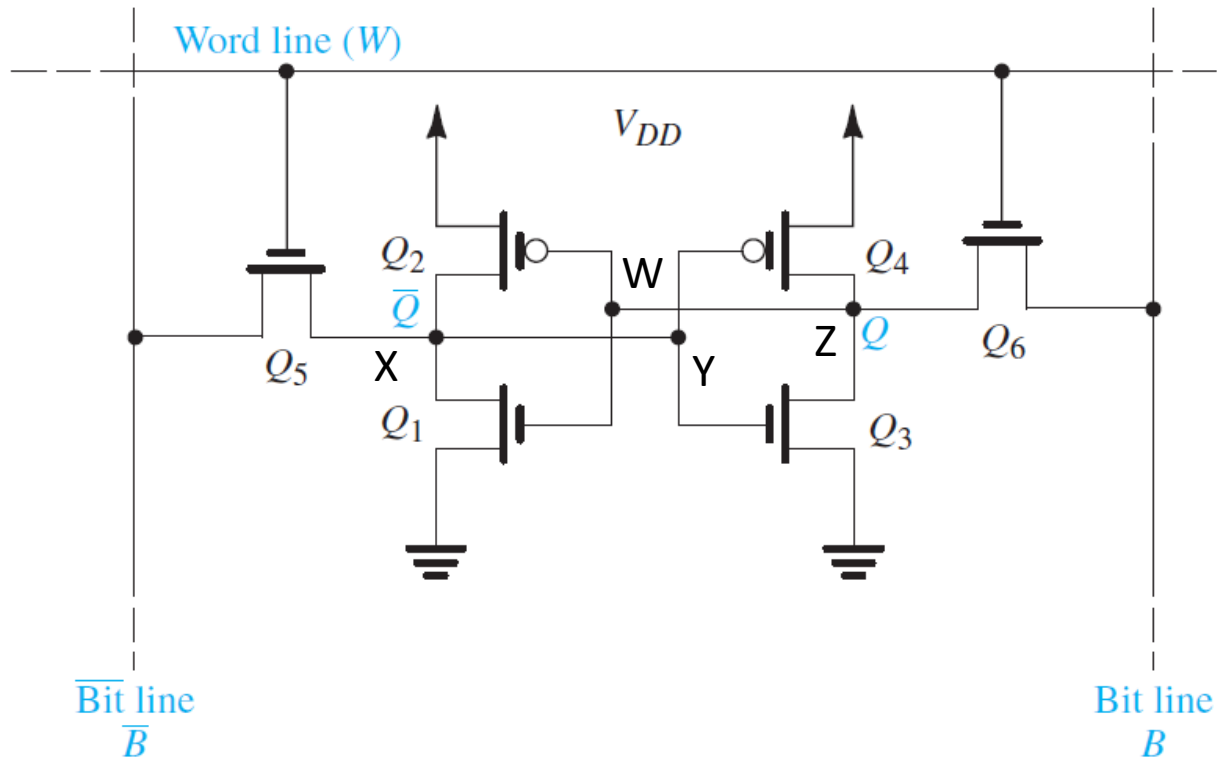

**Figure 16.12** A CMOS SRAM memory cell.

The access transistors,  $Q_5$  &  $Q_6$ , are turned on when the word line is selected

## Static Memory (SRAM) Cell

a flip-flop

 


Figure 16.12 A CMOS SRAM memory cell.

## The Read Operation

Assume that the cell is storing a “1”,  
 $Q = V_{DD}$ ,  $\bar{Q} = 0$

Precharge: raise the bitline,  $B = \bar{B} = V_{DD}$


Turn on  $Q_5$  and  $Q_6$

Current  $I_5$  flow through  $Q_5$  into  $C_{\bar{Q}}$

$v_{\bar{Q}}$  rises,  $Q_1$  conducts,


Reach equilibrium when  $v_{\bar{Q}} = V_{\bar{Q}}$ ,  $I_5 = I_1$

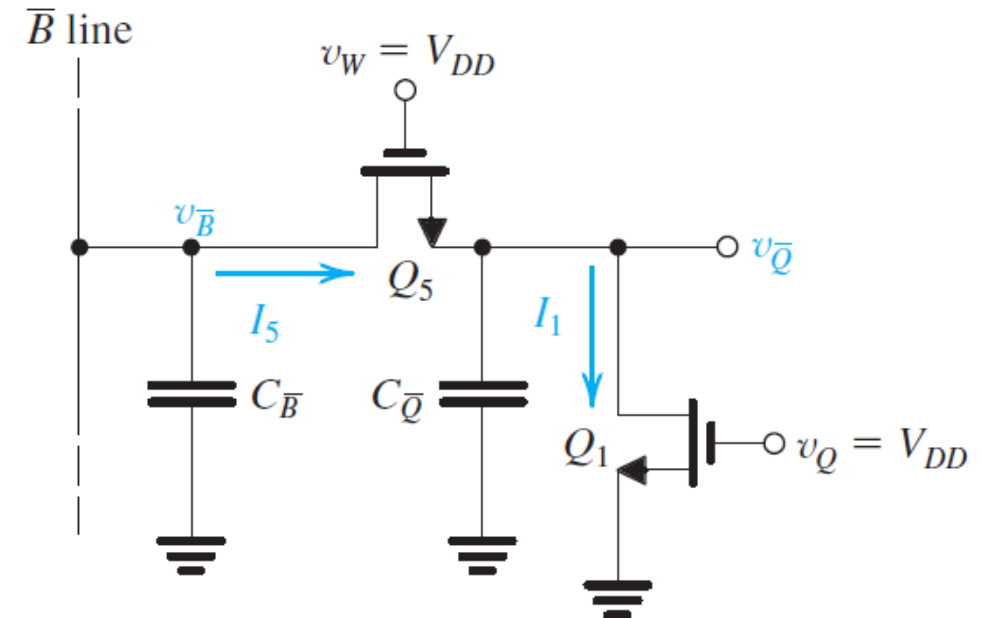the sense amplifier detects a minimum decrement  $\Delta V$  as the presence of “1”.



## Static Memory (SRAM) Cell

a flip-flop

 

## The Read Operation

Assume that the cell is storing a “1”,  
 $Q = V_{DD}$ ,  $\bar{Q} = 0$

Precharge: raise the bitline,  $B = \bar{B} = V_{DD}$


Turn on  $Q_5$  and  $Q_6$

Current  $I_5$  flow through  $Q_5$  into  $C_{\bar{Q}}$

$v_{\bar{Q}}$  rises,  $Q_1$  conducts,



Reach equilibrium when  $v_{\bar{Q}} = V_{\bar{Q}}$ ,  $I_5 = I_1$

 the sense amplifier detects a minimum decrement  $\Delta V$  as the presence of “1”.



## Static Memory (SRAM) Cell

a flip-flop

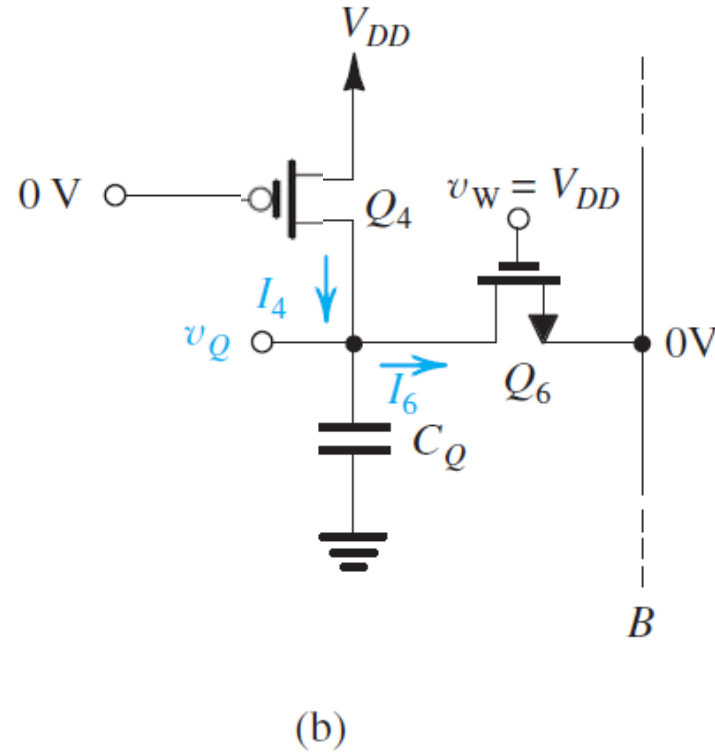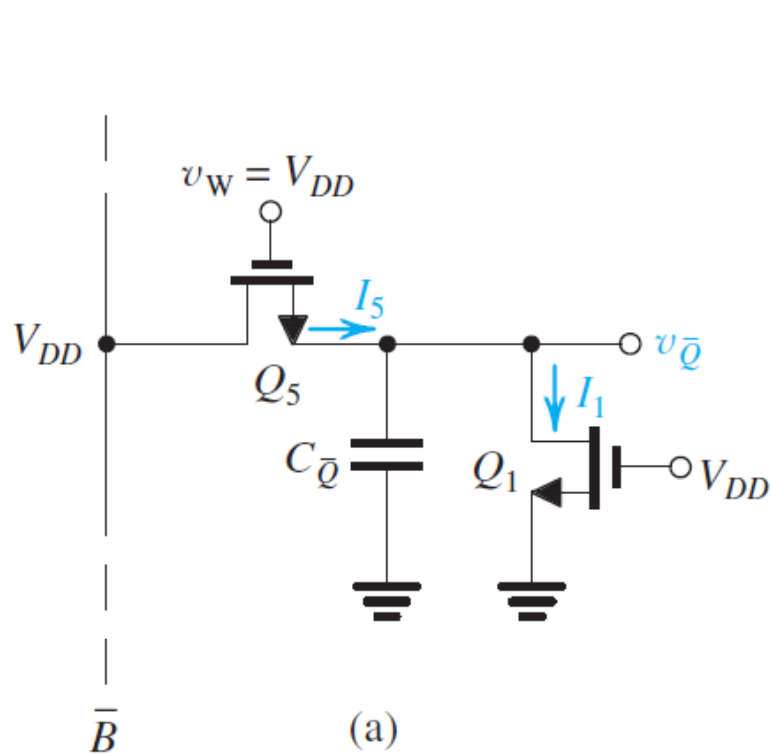

## The Write Operation

Assume that the cell is storing a “1”,  
 $v_Q = V_{DD}$ ,  $v_{\bar{Q}} = 0$

To write a “0”

$$B = 0, \bar{B} = V_{DD}$$

Select a cell,

$$v_W = V_{DD}$$

As  $Q_6$  turns on,  $C_Q$  discharge,

$v_Q$  begins to fall,

$Q_4$  conducts,


Equilibrium is reached when  $I_4 = I_6$ .

$$v_Q < V_{tn}$$

Due to regeneration, the cell is  
toggled to “0” state.

## Dynamic Memory (DRAM) Cell

a bit, 0 or 1, low or high voltage

 

When the cell is storing a 1, the capacitor is charged to  $V_{DD}$ ;  
when a 0 is stored, the capacitor is discharged to zero volts

### one-transistor cell

 


Figure 16.18 The one-transistor dynamic RAM (DRAM) cell.



How the capacitor can be charged to the full supply voltage  $V_{DD}$ ?

a write-1 operation:

Word line =  $V_{DD} + V_t$

Bit line =  $V_{DD}$

Start charging  $C_S$

$C_S$  will reach  $V_{DD}$


Refresh:

The cell content is read,

the data bit is rewritten,

*restoring* the capacitor voltage to its proper value

refresh operation must be performed every 5 ms to 10 ms.

 

**Figure 16.18** The one-transistor dynamic RAM (DRAM) cell.



**Read operation:**

the bit line is precharged to  $V_{DD}/2$ .

Assume a “1” is stored,

$$V_{CS} = V_{DD}$$

Due to charge conversation,

$$C_S V_{CS} + C_B \frac{V_{DD}}{2} = (C_B + C_S) \left( \frac{V_{DD}}{2} + \Delta V \right)$$

where  $\Delta V$  is the change in the voltage on the bit line


$$\Delta V(1) \simeq \frac{C_S}{C_B} \left( \frac{V_{DD}}{2} \right)$$

If  $V_{DD} = 1.8$  V,  $\Delta V(1)$  will be +90 mV,

$\Delta V(0)$  will be about -90 mV

*Read is destructive,*

## Read operation

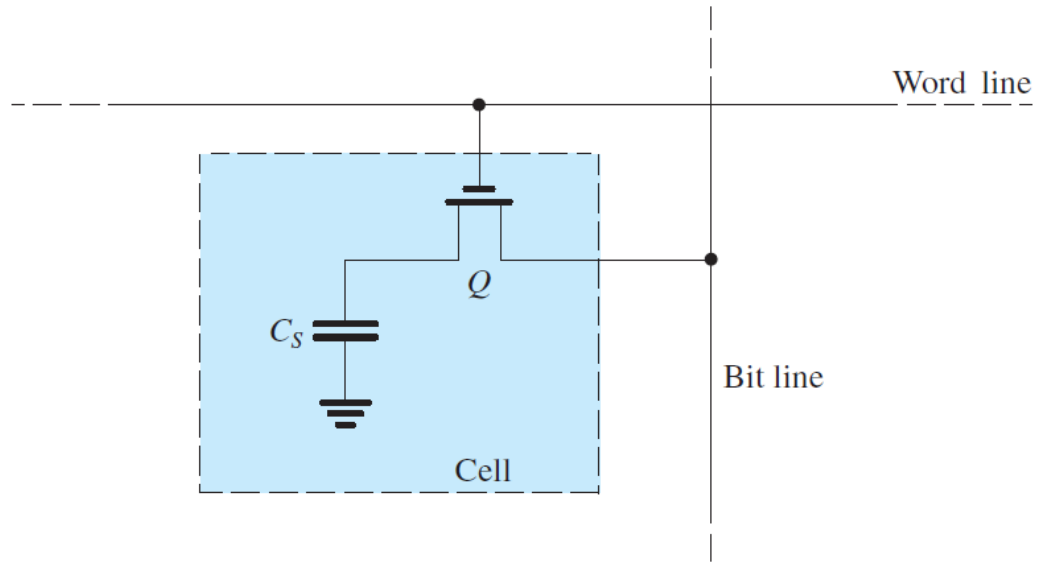

**Figure 16.18** The one-transistor dynamic RAM (DRAM) cell.

### Read operation:

the bit line is precharged to  $V_{DD}/2$ .

Assume a “1” is stored,

$$V_{CS} = V_{DD}$$

Due to charge conversation,

$$C_S V_{CS} + C_B \frac{V_{DD}}{2} = (C_B + C_S) \left( \frac{V_{DD}}{2} + \Delta V \right)$$

where  $\Delta V$  is the change in the voltage on the bit line

$$\Delta V(1) \simeq \frac{C_S}{C_B} \left( \frac{V_{DD}}{2} \right)$$



*Read is destructive,*

$C_S$  will be no longer  $V_{DD}$ ,

$\Delta V$  is amplified by the column sense amplifier


This amplified signal will restore  $C_S$  to  $V_{DD}$

All the cells in the selected row are refreshed.

# Ferroelectric RAM
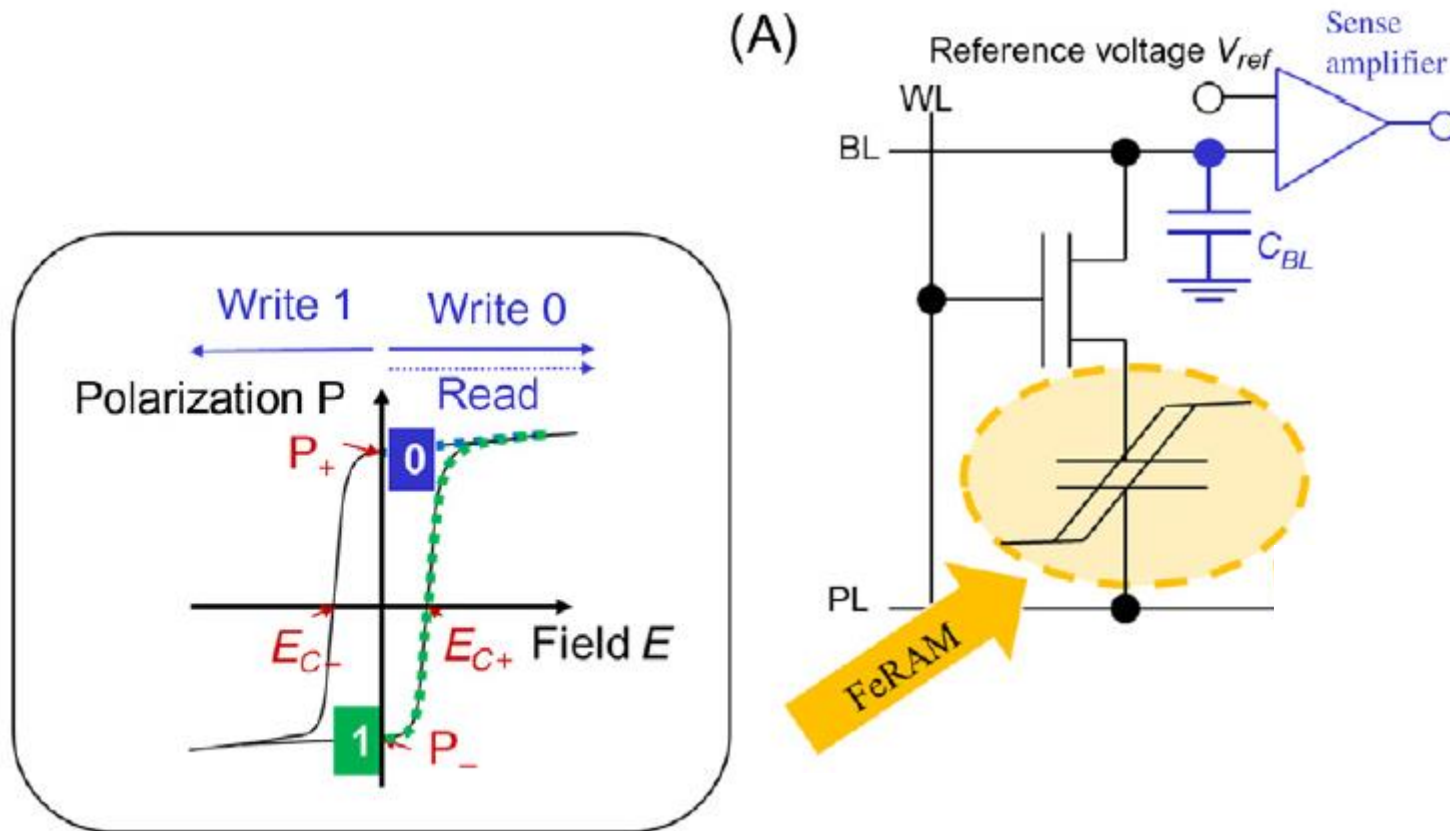
## non-volatile random-access memory

a memory cell is the one transistor - one capacitor (1T-1C) approach that is comparable with a DRAM where the capacitor dielectric is replaced by the **ferroelectric**






How does a ferroelectric random-access memory (FeRAM) work?



Thank you!

 

**Figure 15.5** The  $i_D-v_{GS}$  characteristic of a short-channel NMOS transistor operating at  $v_{DS} > V_{DSsat}$ . Observe the quadratic and the linear portions of the characteristic. Also note that in the absence of velocity saturation, the quadratic curve would continue as shown with the broken line.

Dynamic random-access memory (DRAM)



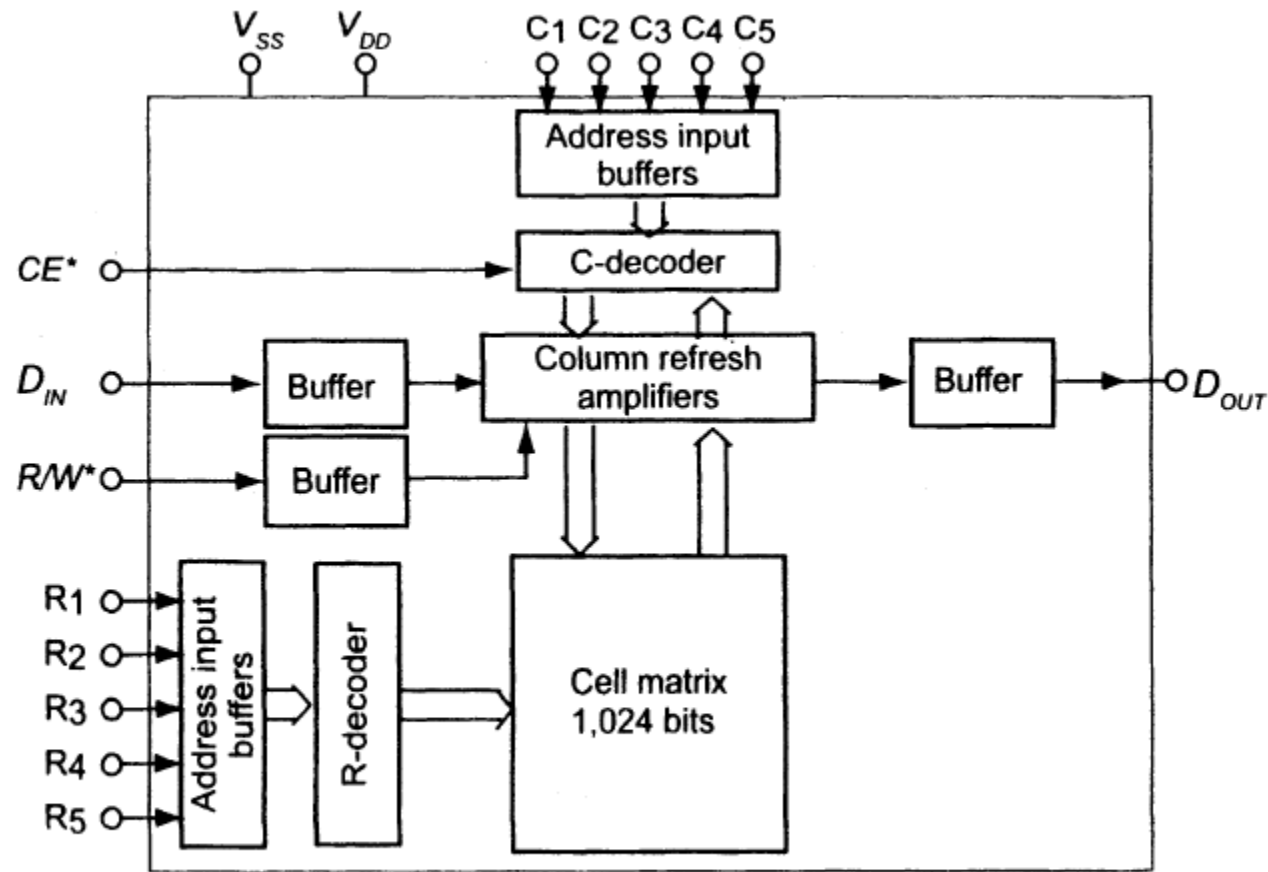



Figure 1.1 1,024-bit DRAM functional diagram.

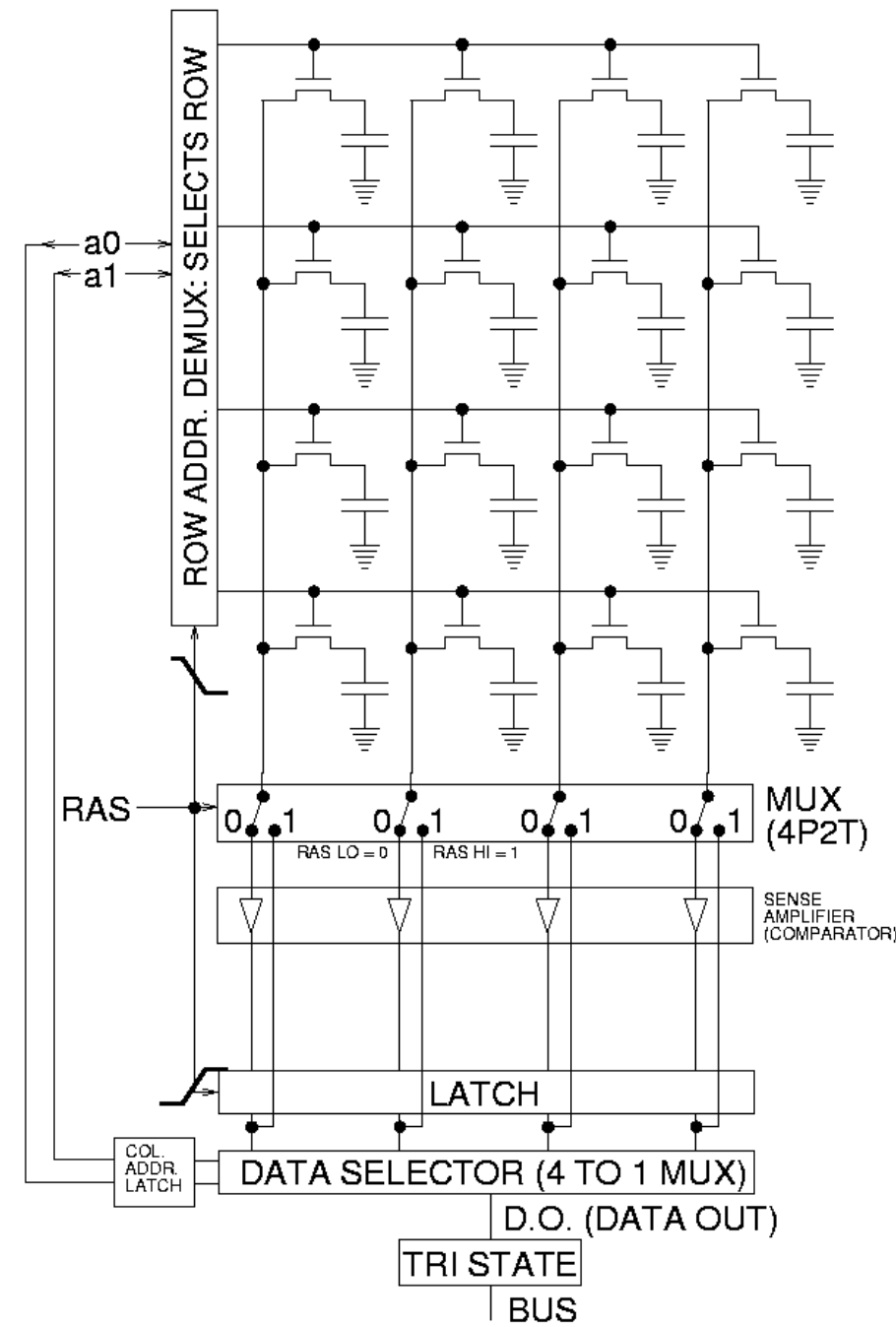

a simple example with a four-by-four cell matrix

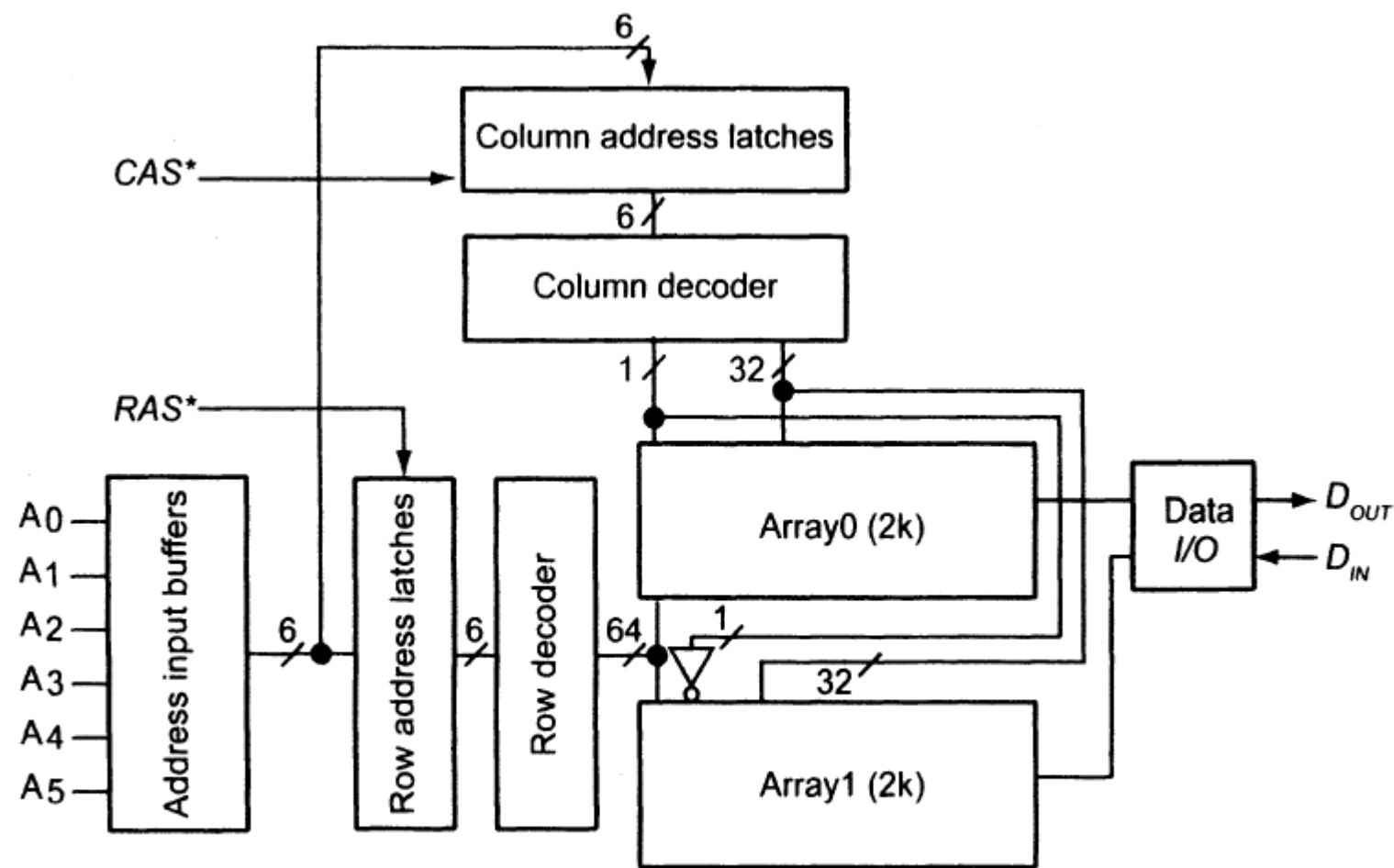

**Figure 1.9** Block diagram of a 4k DRAM.

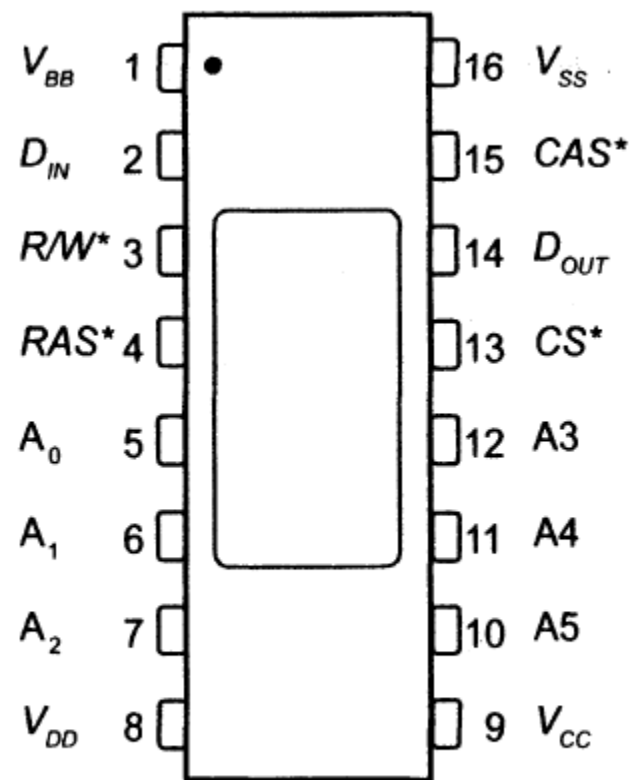

**Figure 1.10** 4,096-bit DRAM pin connections.